

1.1 TITLE OF THE EXPERIMENT.

Inverting amplifier, non inverting amplifier & Voltage follower

1.2 AIM OR OBJECTIVE

To design and implement a Voltage series, shunt feedback amplifier and Voltage follower using op-amp $\mu A 731$.

1.3 LIST OF EQUIPMENTS

S/no	components / device	Specifications	Quantity
1	Regulated DC	0-20V, 2A	02
2	CRO	80Vpp/20MHz	01
3	Power Bank Pack	+12V & -12V	01
4	OP-amp	$\mu A-731$	01
5	function generator	0-1 MHz	01
6	Resistor	10k $\frac{1}{2}$ watt CFR	02
		1k $\frac{1}{2}$ watt CFR	02
7	BNC probes	—	02
8	Wires	—	assorted

1.4 THEORETICAL BACKGROUND

For Inverting amplifiers.

This is most widely used of all the op-amp circuits. The output V_o is fed back to the input through the R_f -in network as shown in figure where R_f is the feedback resistor. The input signal V_i is applied to inverting input terminal through R_{in} and non-inverting input terminal of op-amp is grounded. The output V_o is given by

$$V_o = V_i (-R_f/R_{in})$$

where, the gain of amplifier is $-R_f/R_{in}$

The negative sign indicates a phase shift of 180° between V_i & V_o . effective input impedance is R_i . An inverting amplifier uses negative feedback to invert and amplify a voltage. The R_{in} , R_f resistors network allows some of the output signal to be returned to the inverting input. Since output is 180° out of phase, this amount is effectively subtracted from the input.

For non inverting amplifier.

In case of non-inverting amplifier input is applied to non-inverting terminal of opamp, the gain is calculated by.

$$V_o/V_{in} = 1 + R_f/R_i$$


Voltage follower.

Voltage follower is one of the simplest uses of an operational amp where the output voltage is exactly same as the input voltage applied to the circuit. Gain is Unity.

1.5 DESIGN

Inverting amplifier design.


$$\text{Voltage Gain} = -R_f/R_i$$

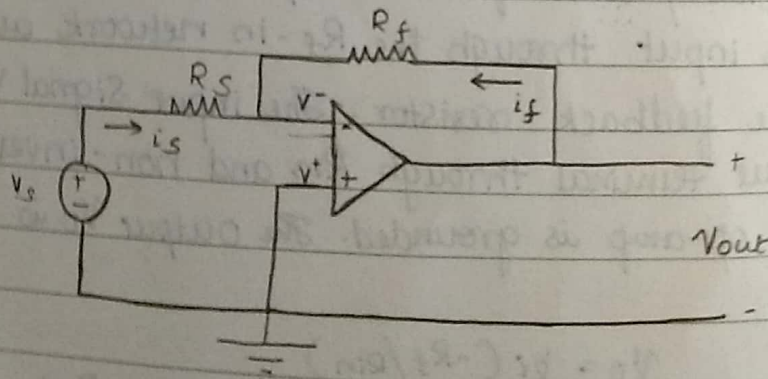

INVERTING AMPLIFIER

Non Inverting Amplifier


$$\text{Voltage Gain} = (1 + R_f/R_i)$$

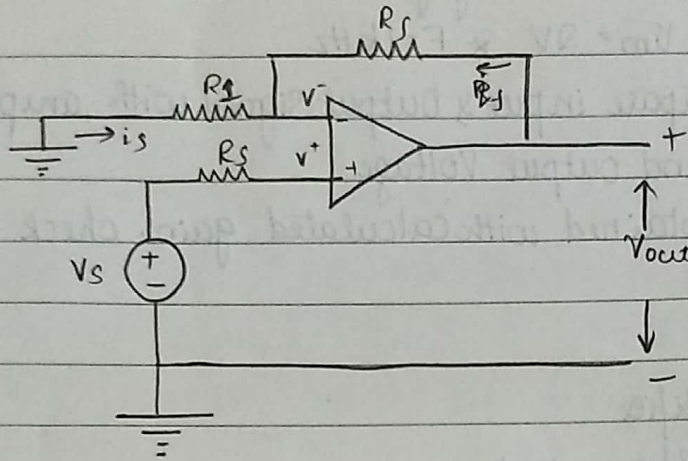

NON INVERTING AMPLIFIER.

for Voltage follower
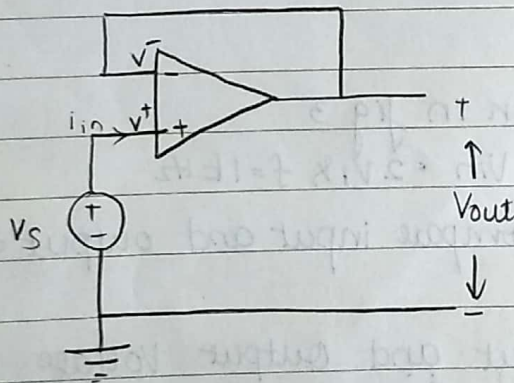
$$\text{Gain} = V_o/V_{in} = 1 \text{ (unity)}$$



VOLTAGE FOLLOWER

1.6. STEP BY STEP PROCEDURE

For inverting amplifier

- connect the circuit as shown in fig 1
- Supply sinusoidal input $V_m = 2V$ & $F = 1kHz$
- check Output on CRO, compare input & Output Signal with amplitude & frequency
- Plot the graph for input and output Voltage
- compare practical gain obtained with calculated gain. check phase of input and output signal

For non-inverting amplifier

- connect the circuit as shown in fig 2
- Supply sinusoidal input $V_{in} = 2V$ & $f = 1kHz$
- check Output on CRO, compare input and output signal with amplitude and frequency
- Plot the graph for input and Output Voltage
- compare practical gain obtained with calculated gain. check phase of input and output signal

For Voltage follower

- connect circuit as shown in fig 3
- Supply sinusoidal input $V_{in} = 2V$ & $f = 1kHz$
- check Output on CRO, compare input and output signal with amplitude & frequency
- Plot the graph for input and output Voltage.
- compare practical gain obtained with calculated gain.

1.7 TABLE OF OBSERVATIONS

for inverting amplifier.

S/no.	V_i	V_o	observed Gain	calculated Gain
1	0.9	8	- 8.88	10
2	1.9	18.5	- 9.73	10

for non-inverting amplifier

S/no	V_i	V_o	Observed Gain	calculated Gain
1	1	9	9	10.11
2	2	19.6	9.8	10.11

for Voltage follower.

S/no	V_i	V_o	observed Gain	calculated Gain
1	1.7	1.8	1.05	1
2	2.7	2.85	1.05	1

1.8 SPECIMEN CALCULATIONS.

for inverting

$$\text{Gain} = -R_f/R_i$$

Let required gain be 10

$$R_i = 1k\Omega$$

$$\therefore R_f = 10k\Omega$$

for non-inverting.

$$\text{Gain} = 1 + R_f/R_i$$




$$\text{Gain required} = 11$$

Assume $R_1 = 1k\Omega$
 $\therefore R_f = 10k\Omega$

Voltage follower

Gain = 1.

1.9 NATURE OF GRAPH.

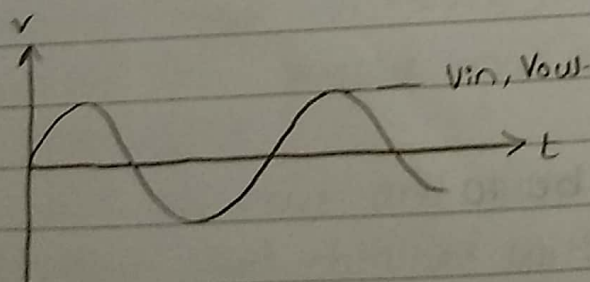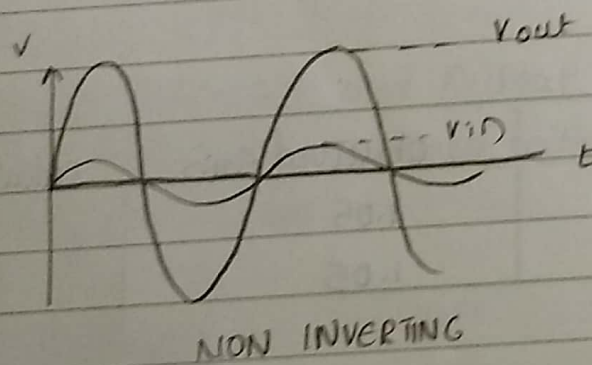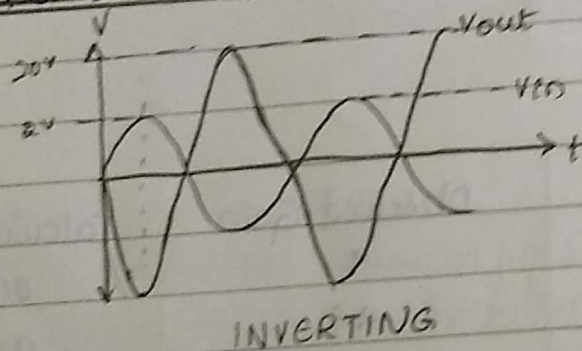

NO CONCLUSION OF THE EXPERIMENT.

Result & Discussion.

experimental Set up of Inverting amplifier gives a signal out of phase by 180° . The Gain is nearly 10.

For non inverting, the Output is in phase Gain is nearly 10.

for Voltage follower.

the Gain is almost 1 and the output is in phase

CONCLUSION

Op-amp is a device with 2 input terminals and One Output terminal, with input and Output Signal is plotted and observed gain is calculated, which in turn is Verified with calculated gain


EXPERIMENT NO.:

DATE:

SCALE:

X-axis: $1\text{ cm} = 1\text{ ms}$

Y-axis: $1\text{ cm} = 1\text{ V}$

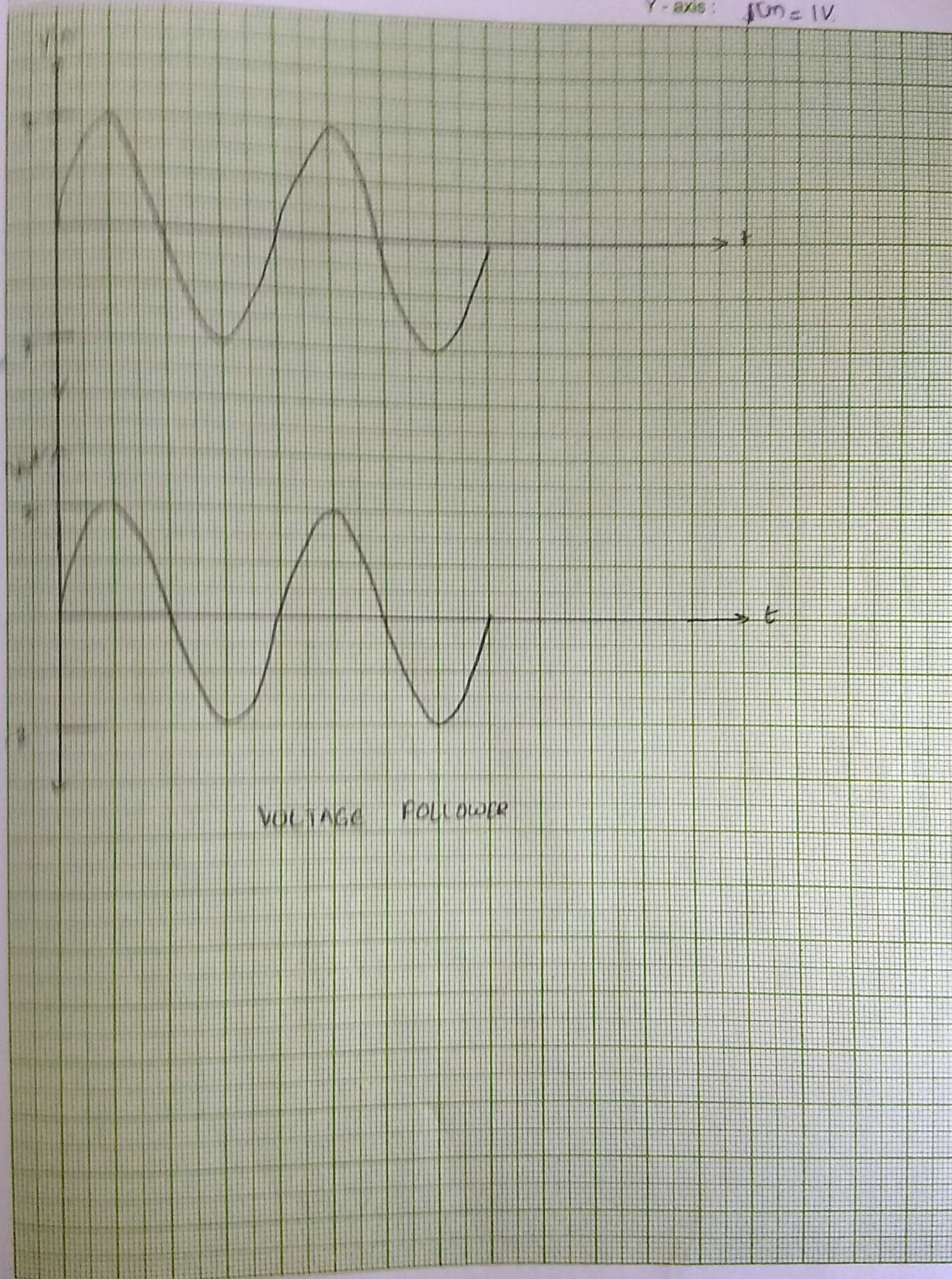

VOLTAGE FOLLOWER


EXPERIMENT NO.:

DATE V_{in}, V_o


SCALE:

X-axis: $4V = 1ms$

Y-axis: $1V = 5cm$

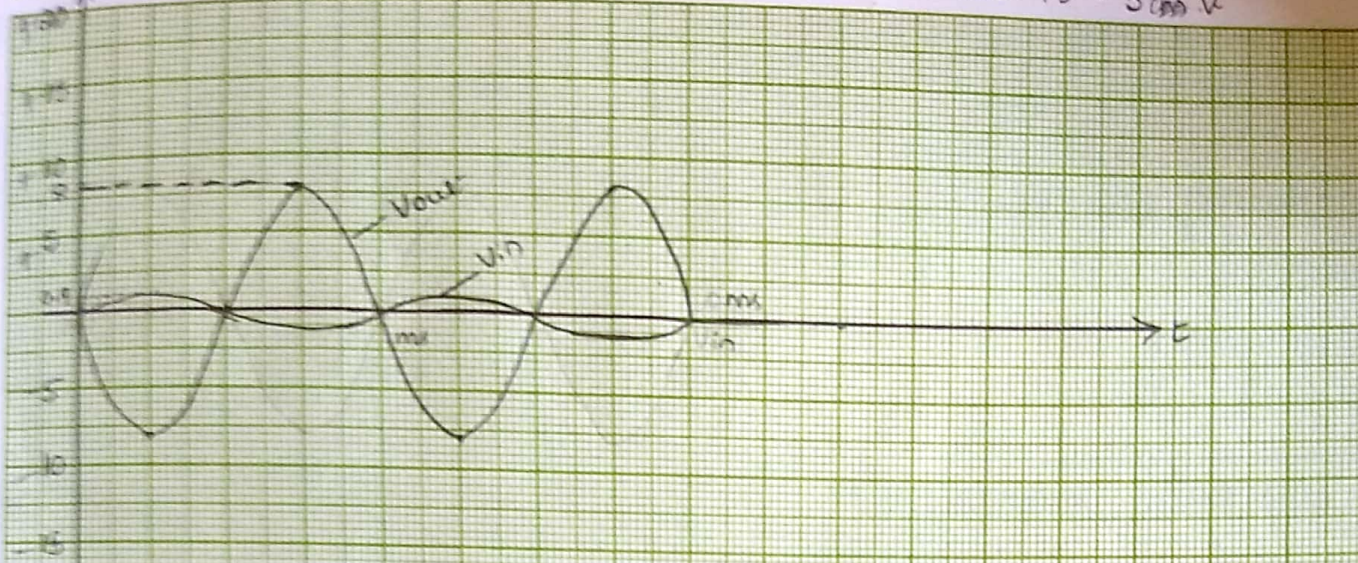

INVERTING AMPLIFIER

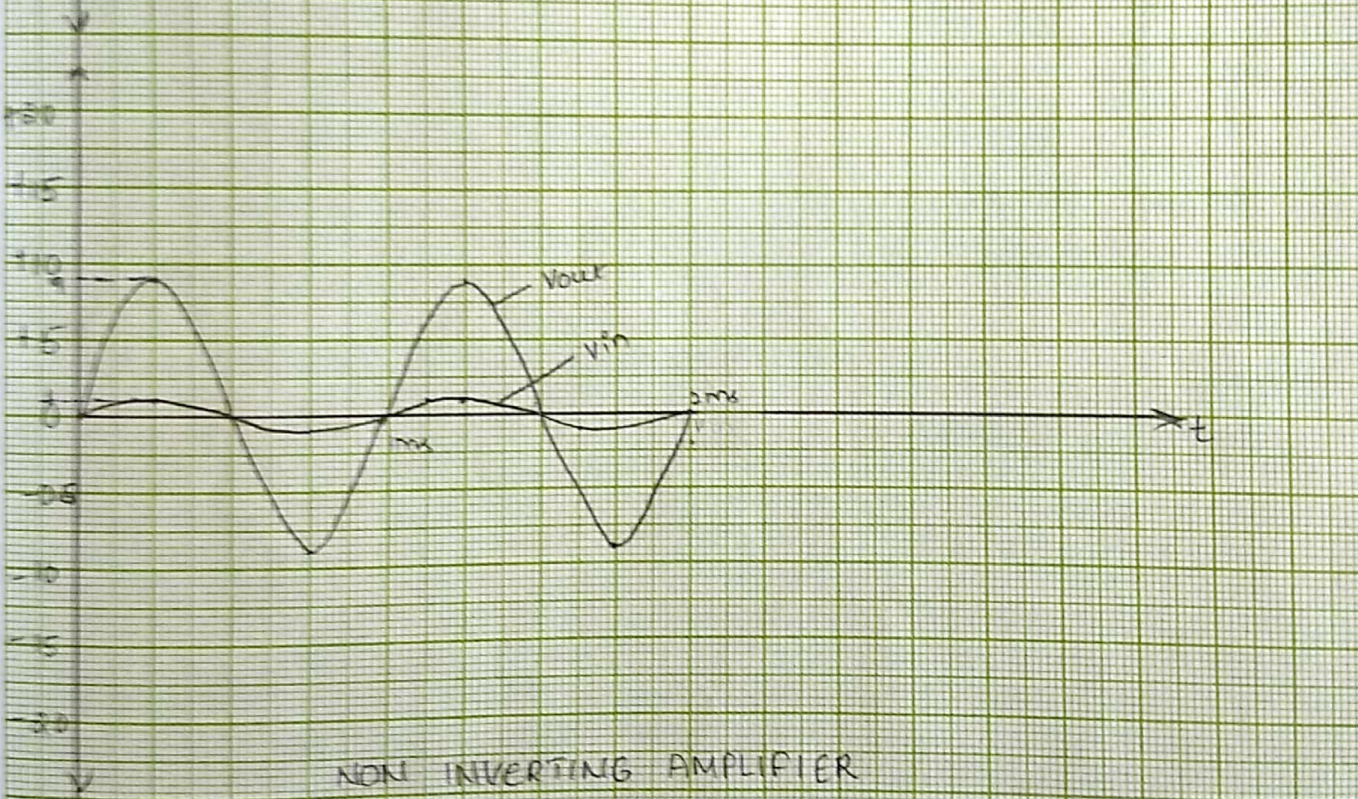

NON INVERTING AMPLIFIER

2.1 TITLE OF THE EXPERIMENT

zero crossing detector, Schmitt trigger, precision rectifier.

2.2 AIM OF THE EXPERIMENT

To design and implement ZCD, Schmitt trigger and precision rectifier.

2.3 LIST OF EXPERIMENTS

Sl no.	Components / Devices	Specifications	Quantity.
1.	Regulated Dc	0-20V, 2A	2
2.	CRO	80Vpp / 20MHz	1
3.	Power Pack	+12V & -12V.	1
4.	Op amplifier	μA-741	2
5.	Function generator	0-1 MHz	1
6	Resistors	1k, 1/4 watt	4
7		5k, 1/4 watt	3
8	BNC probes	-	3
9	Single strand Wires.	-	assorted
	Diodes	1N4001	2.


2.4. DESIGN.

a) Zero crossing Detector

Sine wave to Square Wave converter.

$$\text{when } V_{in} = +V_i \Rightarrow V_o = -V_{sat}$$
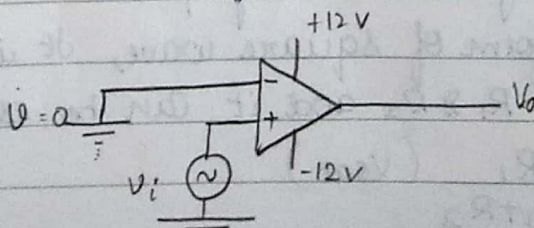
$$V_{in} = -V_i \Rightarrow V_o = +V_{sat}$$



b) Schmitt trigger.


$$V_{thp} = \frac{R_1}{R_1 + R_2} (V_{sat})$$

$$V_{ltp} = \frac{R_1}{R_1 + R_2} (-V_{sat})$$


let us consider $R_1 = 1k\Omega$

assume $V_{thp} = -V_{ltp} = 2V$ so w.k.t $V_{sat} = 12V$

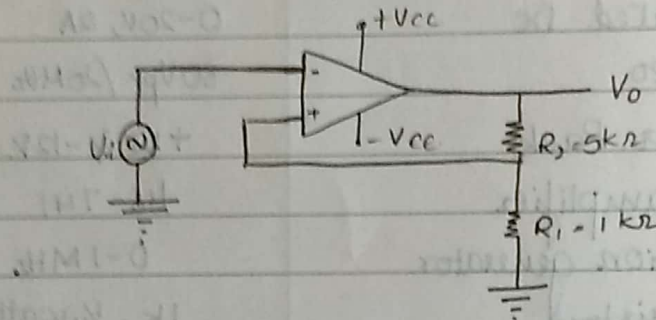$\therefore$ from the above equations we get $R_2 = 5k\Omega = 4.7k\Omega$



c) Precision Rectifier

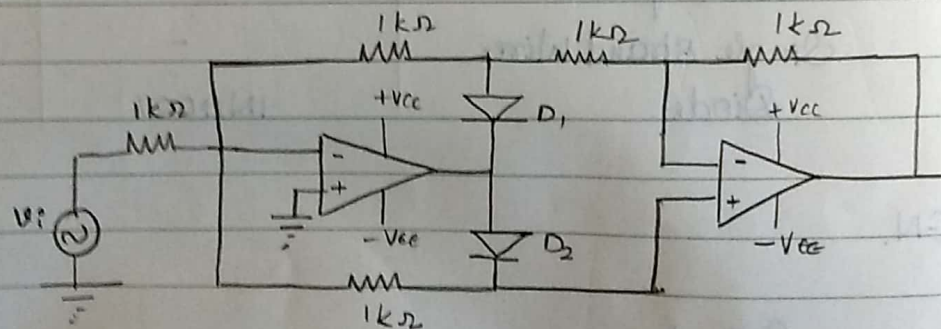2.5. STEP BY STEP PROCEDURE

- connect the components as shown in the figure.
- Give the input Sine wave from inverting pin.
- Output should be in the form of square wave, it is magnitude depends on the resistors R_1 & R_2 and it can be estimated using the formula $V_{thp} = \frac{R_1}{R_1 + R_2} (V_{sat})$

for Zero crossing Detector.

Make connections as shown in fig.

Give input voltage (sine wave) and output will be square wave.

Magnitude of output signal will be $+V_{cc}$ & $-V_{ee}$

for Precision Rectifier.

Make connections as shown in fig.

Give the input sine wave (AC) from inverting pin

Output will be half rectified

2.6. TABLE OF OBSERVATION.

Zero crossing Detector.

S/no.	V_{in}	V_{out}	frequency (Hz)
1	1.4V	9V	1kHz
2	1.6V	9V.	1kHz

Schmitt trigger.

S/no	V_{in}	frequency	V_{LP}	V_{UP}
1	1V	1kHz	6V	+12V.
2				

Precision rectifier.

S/no.	V_{in}	freq.	time period	output voltage	o/p time
1	1.4	1kHz	1	1	1
2	1.5	1kHz	1	1.5	1

2.7. SPECIMEN CALCULATION.

Schmitt trigger

$$V_{thp} = \frac{R_1}{R_1 + R_2} (+V_{sat})$$

$$V_{thp} = \frac{R_1}{R_1 + R_2} (-V_{sat})$$

assume $V_{upp} = -V_{thp} = 2V$ & $R_1 = 1k\Omega$



We know that $V_{cc} = -V_{ss} = 12V$

$\therefore$ from the eqⁿ. $= \frac{1k}{1k + R_2} (12)$



$$R_2 = 5k\Omega$$

2.8 NATURE OF GRAPH.



Zero crossing Detector

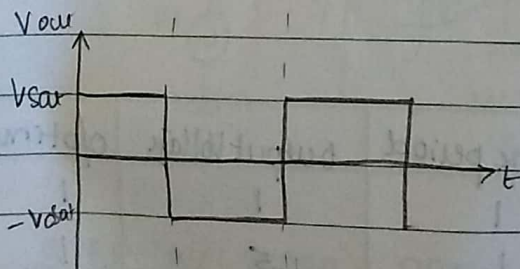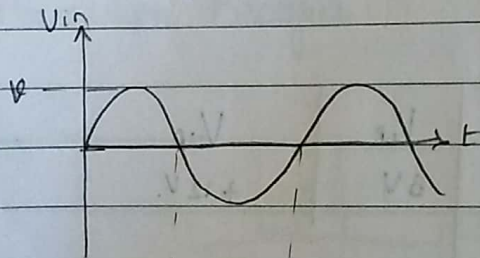

Schmitt trigger.

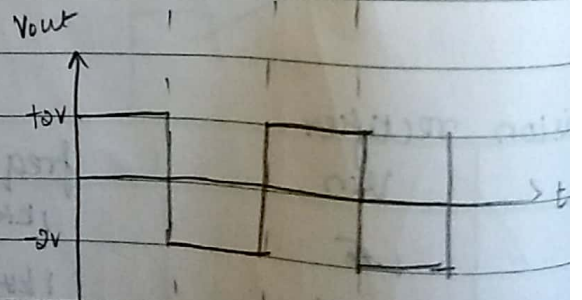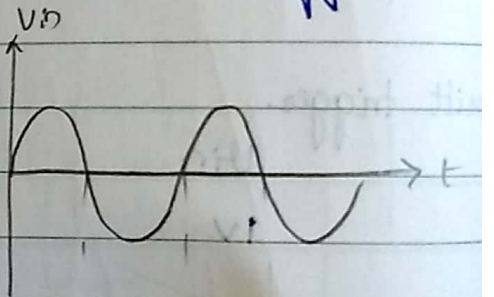

Precision Rectifier

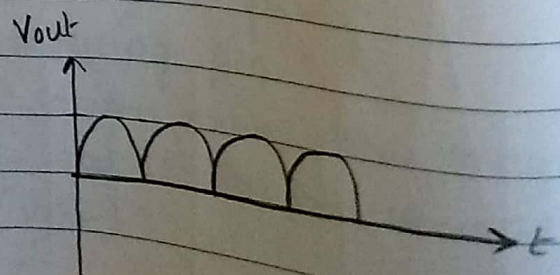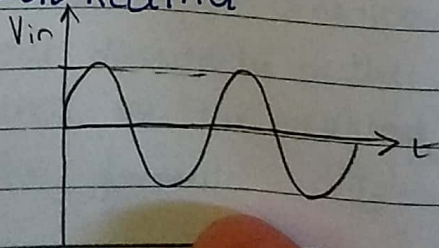

We have successfully implemented the ZCD, Schmitt trigger and precision rectifier and got the results similar to the expected ones


EXPERIMENT NO.:

DATE:

SCALE:

X-axis: $1\text{cm} = 1\text{ms}$

Y-axis: $1\text{cm} = 2.5\text{V}$

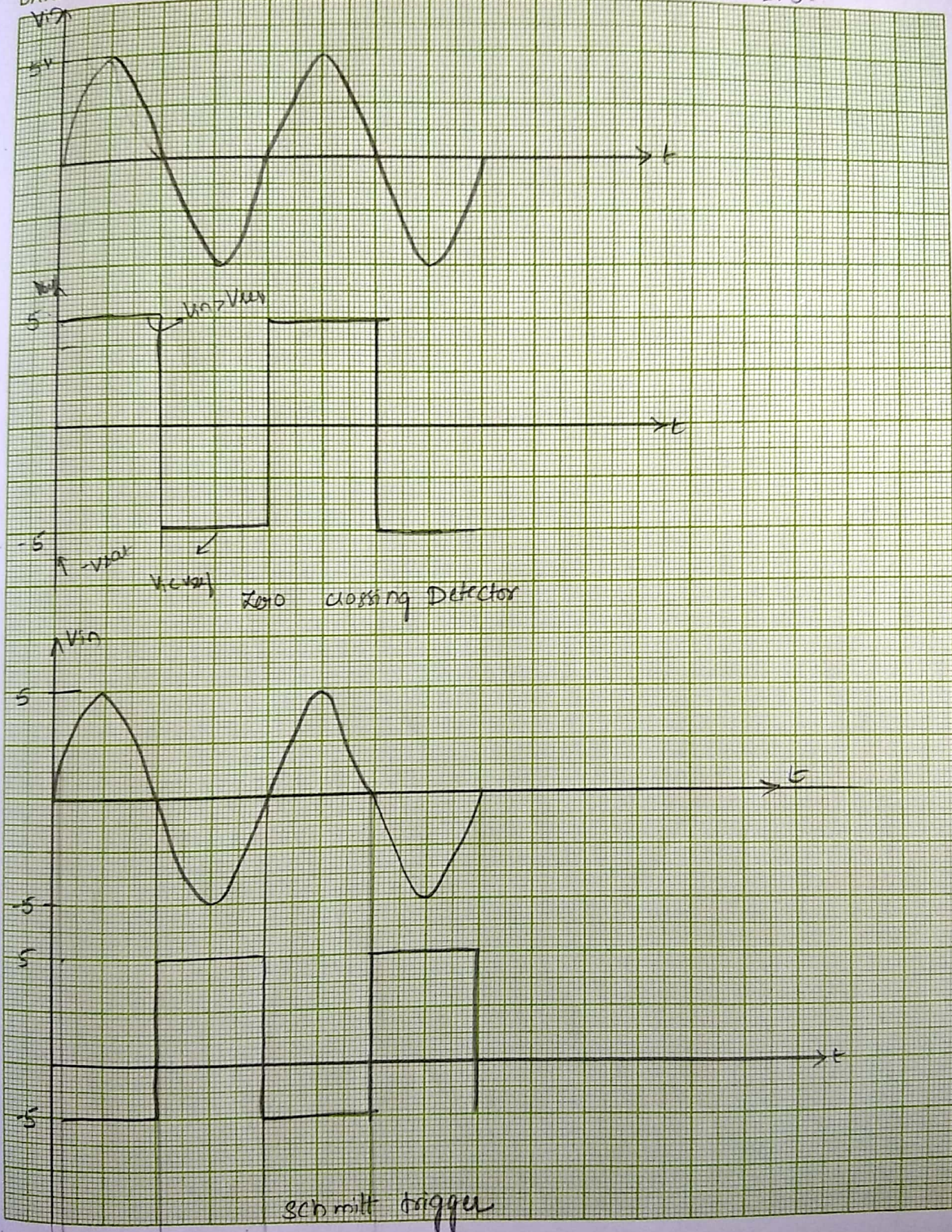


EXPERIMENT NO. :

DATE :

SCALE :

X-axis : 1cm = 1ms

Y-axis : 1cm = 5V

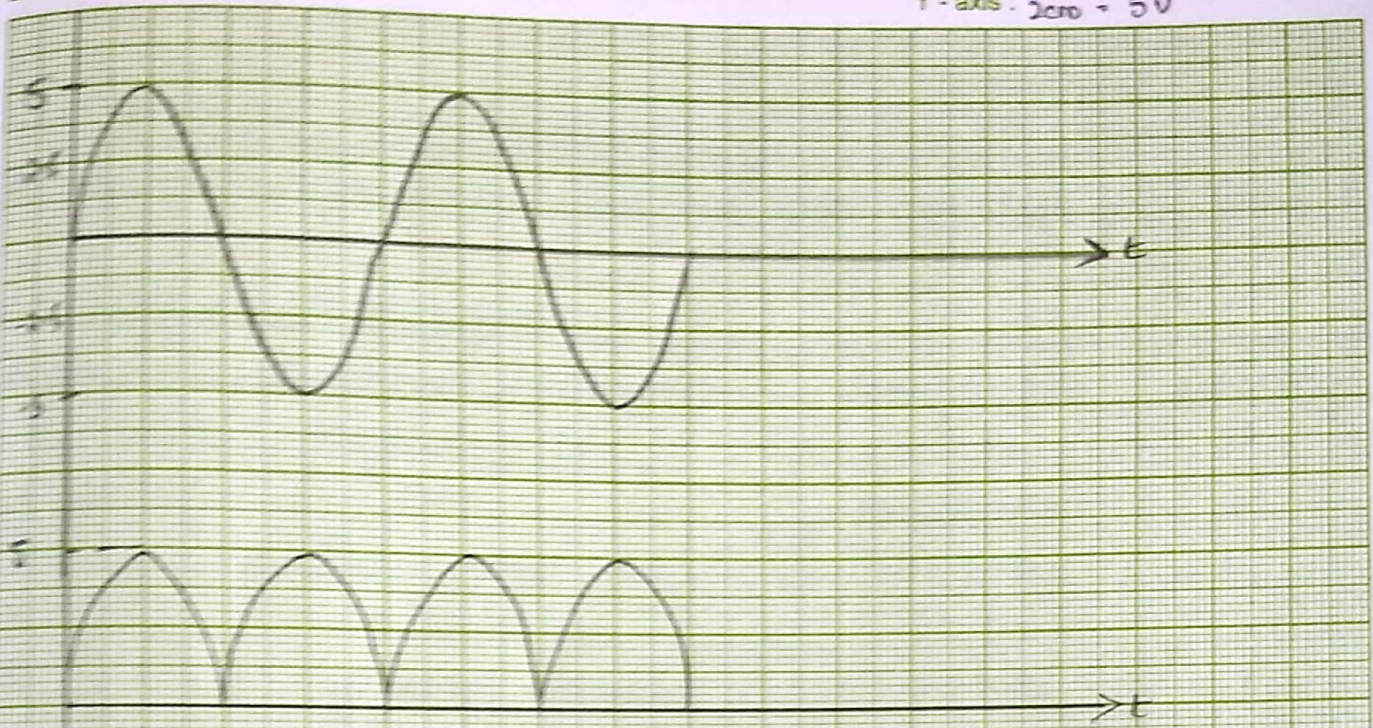

Full wave precision rectifier

3.1 TITLE OF THE EXPERIMENT.

Second Order filters.

3.2. AIM OF THE EXPERIMENT.

To design and implement low pass filter and high pass filter.

3.3. LIST OF COMPONENTS.

S/no	components / equipments	Specifications	Quantity
1	Regulated DC.	0-20V, 2A	2
2.	CRO	80Vpp/20MHz	1
3	Power pack	+12V & -12V	1
4	Op. amplifier	μA-741	1
5.	function generator	0-1 MHz	1
6.	Resistor.	1.5 kΩ	2
		2.2 kΩ	1
		1 kΩ	1
7	capacitors	0.01 μF	2
8.	BNC probes	-	3
9	Wires	-	assorted.

3.4 DESIGN.

$$A_f = 1 + R_f/R_1 \quad \text{consider,}$$

$$f_c = \frac{1}{2\pi \sqrt{R_2 R_3 C_2 C_3}} \quad - (1)$$

$$\text{assume } C_2 = C_3 = C \text{ and } R_2 = R_3 = R$$

∴ (1) becomes.


$$f_c = \frac{1}{2\pi RC} \quad (\text{consider } C = 0.01 \mu F)$$

$$\text{Let } f_c = 10 \text{ kHz} \Rightarrow 10 \times 10^3 = \frac{1}{2\pi R \times 0.01 \times 10^{-6}}$$


$$R = 1.59 \text{ k}\Omega$$

$$\text{Gain, } \frac{R_f}{R_1} + 1 = \frac{1}{2.2} + 1 = 1.45$$

a) Low Pass filters

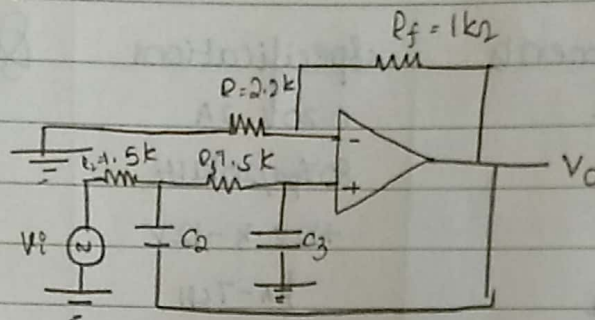

b) High Pass filter

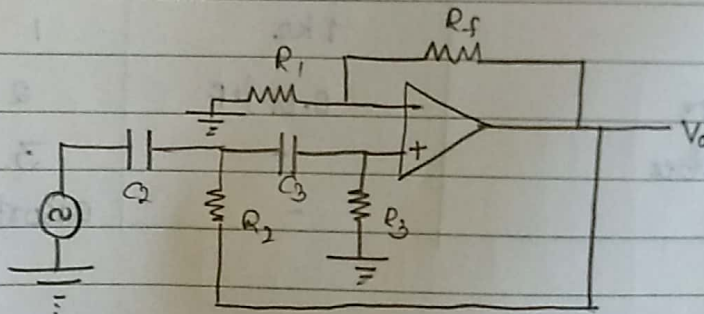

3.5. STEP BY STEP PROCEDURE

a) Low pass filter

- connect the circuit as shown in the fig.
- Increase the input frequency from 100Hz to 10kHz slowly and after the increase rapidly keep i/p Volt constant.
- Note down the output gain
- Draw gain vs frequency graph

b) High pass filter

- Make connections as shown in the fig 2.
- Increase the input frequency rapidly till 10kHz afterwards increase slowly till 1 MHz. Keep V_p Volt constant
- Note down the output gain
- Draw gain V_o frequency graph.

3.6. TABLE OF OBSERVATIONS

S/no	frequency	$V_o(P)(V)$	Gain = V_o/V_{in}	Gain (dB)
1	100 Hz	1.45	1.45	3.227
2	200 Hz	1.45	1.45	3.227
3	300 Hz	1.45	1.45	3.227
4	400 Hz	1.45	1.45	3.227
5	500 Hz	1.45	1.45	3.227
6	600 Hz	1.45	1.45	3.227
7	700 Hz	1.45	1.45	3.227
8	800 Hz	1.45	1.45	3.227
9	900 Hz	1.45	1.45	3.227
10	1 kHz	1.45	1.45	3.227
11	2 kHz	1.45	1.45	3.227
12	3 kHz	1.45	1.45	3.227
13	4 kHz	1.45	1.45	3.227
14	5 kHz	1.4	1.4	2.92
15	6 kHz	1.4	1.4	2.92
16	7 kHz	1.25	1.25	1.938
17	8 kHz	1.2	1.2	1.58
18	9 kHz	1.1	1.1	0.828
19	10 kHz	1.0	1.0	0
20	11 kHz	0.9	0.9	-0.91

S/no	frequency	$V_{ocp}(v)$	$Gain = V_o/V_{in}$	Gain (dB)
21	12 kHz	0.85	0.85	-1.412
22	13 kHz	0.6	0.6	-4.437
23	14 kHz	0.45	0.45	-6.9357
24	15 kHz	0.45	0.45	-6.9352
25	16 kHz	0.4	0.4	-7.959
26	17 kHz	0.4	0.4	-7.959
27	18 kHz	0.4	0.4	-7.959
28	19 kHz	0.25	0.25	-12.041
29	20 kHz	0.25	0.25	-12.041
30	25 kHz	0.2	0.2	-13.979
31	30 kHz	0.1	0.1	-20

b) HIGH PASS FILTER ($V_{in} = 1V_p$)

S/no	frequency	$V_{ocp}(v)$	$Gain = V_o/V_{in}$	Gain (dB)
1	100 Hz	0	0	
2	200 Hz	0	0	
3	300 Hz	0	0	
4	400 Hz	0	0	
5	500 Hz	0	0	
6	600 Hz	0	0	
7	700 Hz	0.1	0.1	-20
8	800 Hz	0.1	0.1	-20
9	900 Hz	0.1	0.1	-20
10	1 kHz	0.1	0.1	-20
11	2 kHz	0.15	0.15	-16.478
12	3 kHz	0.2	0.2	-13.979
13	4 kHz	0.22	0.22	-13.151
14	5 kHz	0.25	0.25	-12.041
15	6 kHz	0.4	0.4	-7.959
16	7 kHz	0.55	0.55	-5.193

Slno	frequency	$V_o(p)(V)$	Gain V_o/V_{in}	Gain (db)
17	8 kHz	0.6	0.6	-4.437
18	9 kHz	0.8	0.8	-1.938
19	10 kHz	0.9	0.9	-0.915
20	11 kHz	0.95	0.95	-0.445
21	12 kHz	1.0	1.0	0
22	13 kHz	1.1	1.1	0.825
23	14 kHz	1.15	1.15	1.214
24	15 kHz	1.2	1.2	1.584
25	16 kHz	1.2	1.2	1.584
26	17 kHz	1.25	1.25	1.938
27	18 kHz	1.3	1.3	2.279
28	19 kHz	1.3	1.3	2.279
29	20 kHz	1.35	1.35	2.606
30	25 kHz	1.4	1.4	2.922
31	30 kHz	1.4	1.4	2.922

3.7. SPECIMEN CALCULATION.

cut off frequency

Gain

$$f_c = \frac{1}{2\pi RC}$$

$$R = 1.5 k\Omega$$

$$C = 0.01 \mu F$$

$$A_u = 1 + \frac{R_f}{R_i}$$

$$R_f = 1 k\Omega$$

$$R_i = 2.2 k\Omega$$

$$= \frac{1}{2\pi \times 1.5 \times 10^3 \times 0.01 \times 10^{-6}}$$


$$= 1 + \frac{7}{2.2}$$

$$f_c = 10.61 \text{ kHz}$$


$$A_v = 1.45$$

3.8. NATURE OF GRAPH

a) low pass filter.

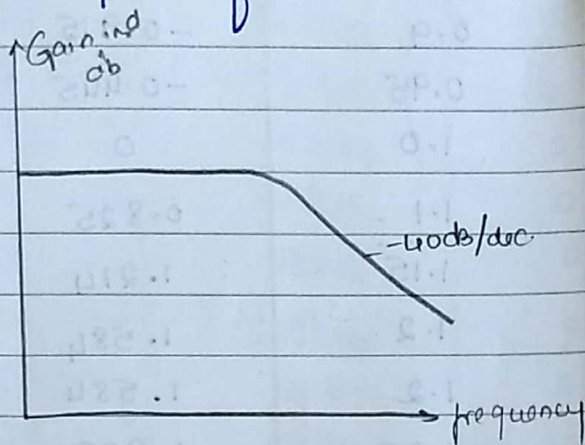

b) High pass filter

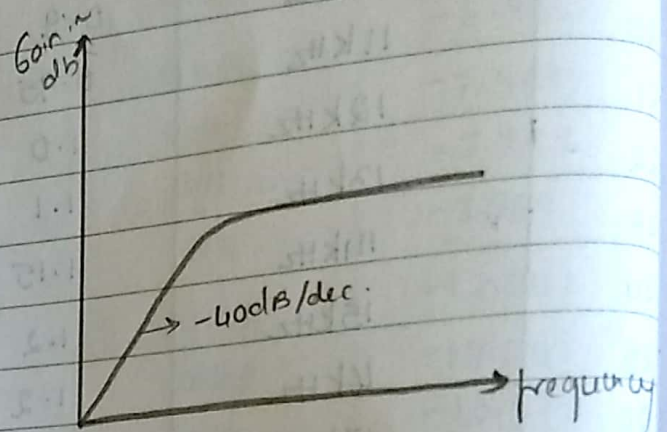3.9. RESULTS AND CONCLUSION.

After the completion of experiment we have concluded that desired outputs are coming but there is a slight error in calculated and observed output. This is because of faulty connections. We are getting cut off frequency as $f_c = 10.61 \text{ kHz}$ when calculated but during observation we are getting as 12 kHz .

4.1. TITLE OF THE EXPERIMENT
Sample and Hold circuits.



4.2. AIM OF THE EXPERIMENT

To design and implement sample and hold circuit using LF398

4.3. LIST OF COMPONENTS

S/no	components/equipment	specification	Quantity
1	Regulated DC		
2	CRO	0-20V, 2A	2
3	function generator	80Vpp/20MHz	1
4	Sample & Hold Ic.	0-1 MHz	2
5	capacitor	LF398	1
6	BNC	01 μ F / 0.1 μ F	1
7	klites		3
			assorted

4.4. DESIGN

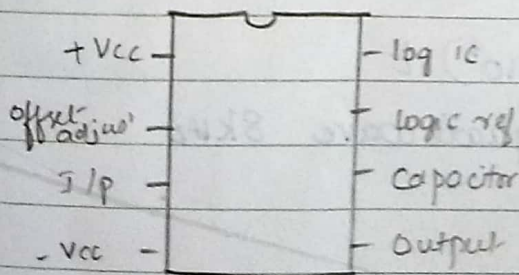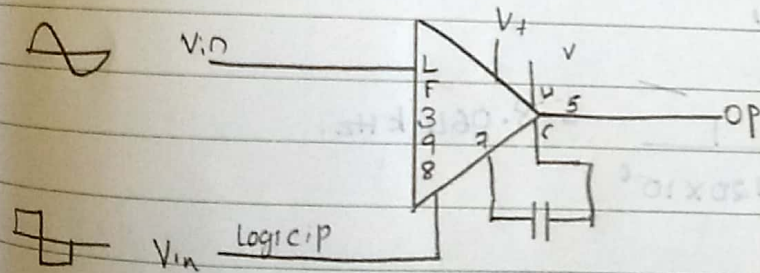

4.5. STEP BY STEP PROCEDURE

- connect as shown in the fig
- Give a Sine wave of $2V_p$ & $1kHz$ from 3rd pin
- Give a Square wave of $2V_p$ & $5kHz$ from pin 5
- Check the Output from CRO.
- Calculate hold and sample time.

4.6. OBSERVATIONS

- Input signal amplitude: $4V_{p-p}$
- d/p signal frequency: $1kHz$
- Logic signal frequency: $8kHz$
- Logic signal amplitude: $4V_{p-p}$
- Amplitude of modulated signal: $4V_{p-p}$
- Hold time of the modulated signal: $60\mu s (T_H)$
- Sample time of the modulated signal: $64\mu s (T_s)$
- $T_{inst} = T_s + T_H$, frequency = $f_s = \frac{1}{T_{inst}}$

$$T_{inst} = 60 + 64$$

$$= 124\mu s.$$


$$f_s = \frac{1}{124 \times 10^{-6}} = 8.064 kHz.$$

4.7. SPECIMAN CALCULATION.

$$V_{in} = 2V_p \sin(2\pi \times 10^3) t$$

$$\text{logic i/p} = 2V_p, \text{ Square wave } 8kHz$$

4.8 NATURE OF GRAPH

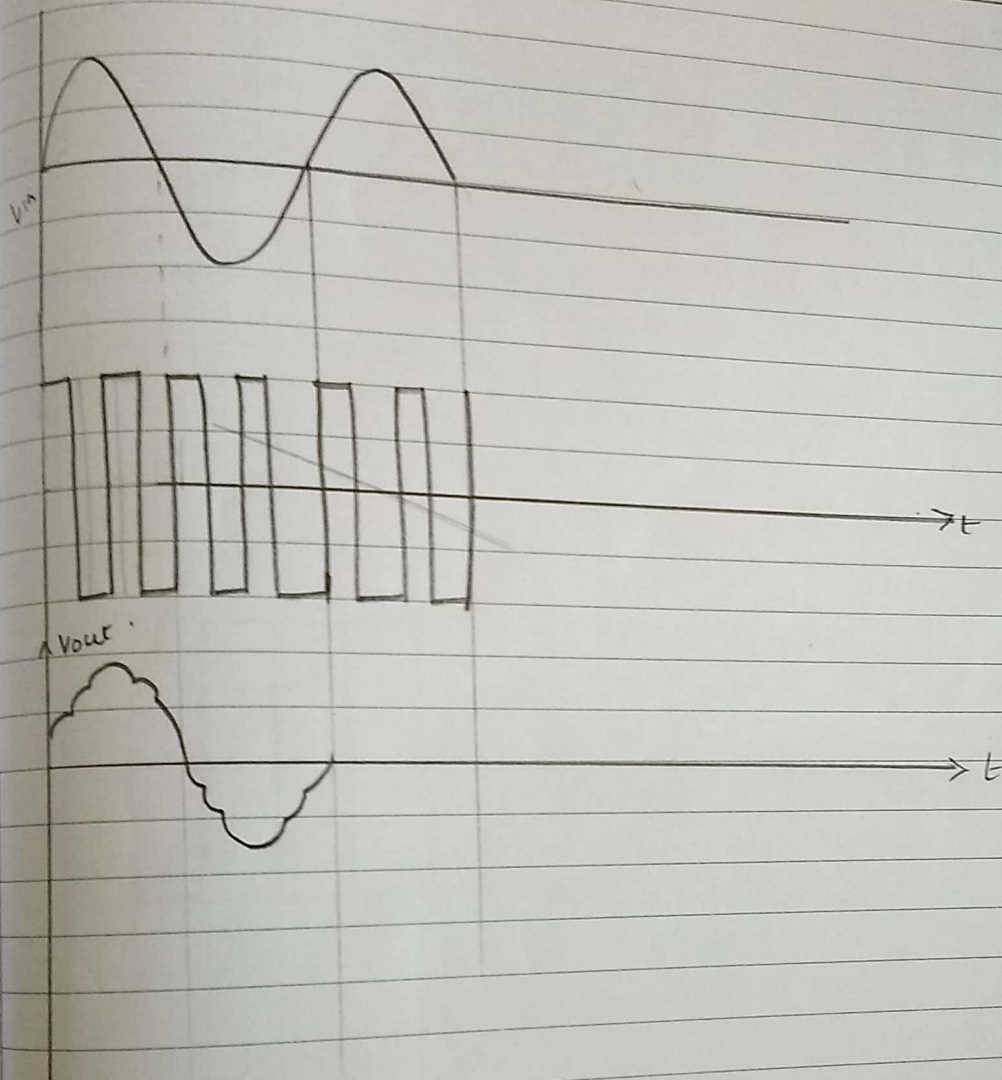

4.9. RESULTS AND CALCULATION.


The circuit that we have designed is working according to our requirement. We are getting the Output as we coated and to improvise the Output just increase the frequency of logic signal input.

EXPERIMENT NO. :

Page No.:

DATE :

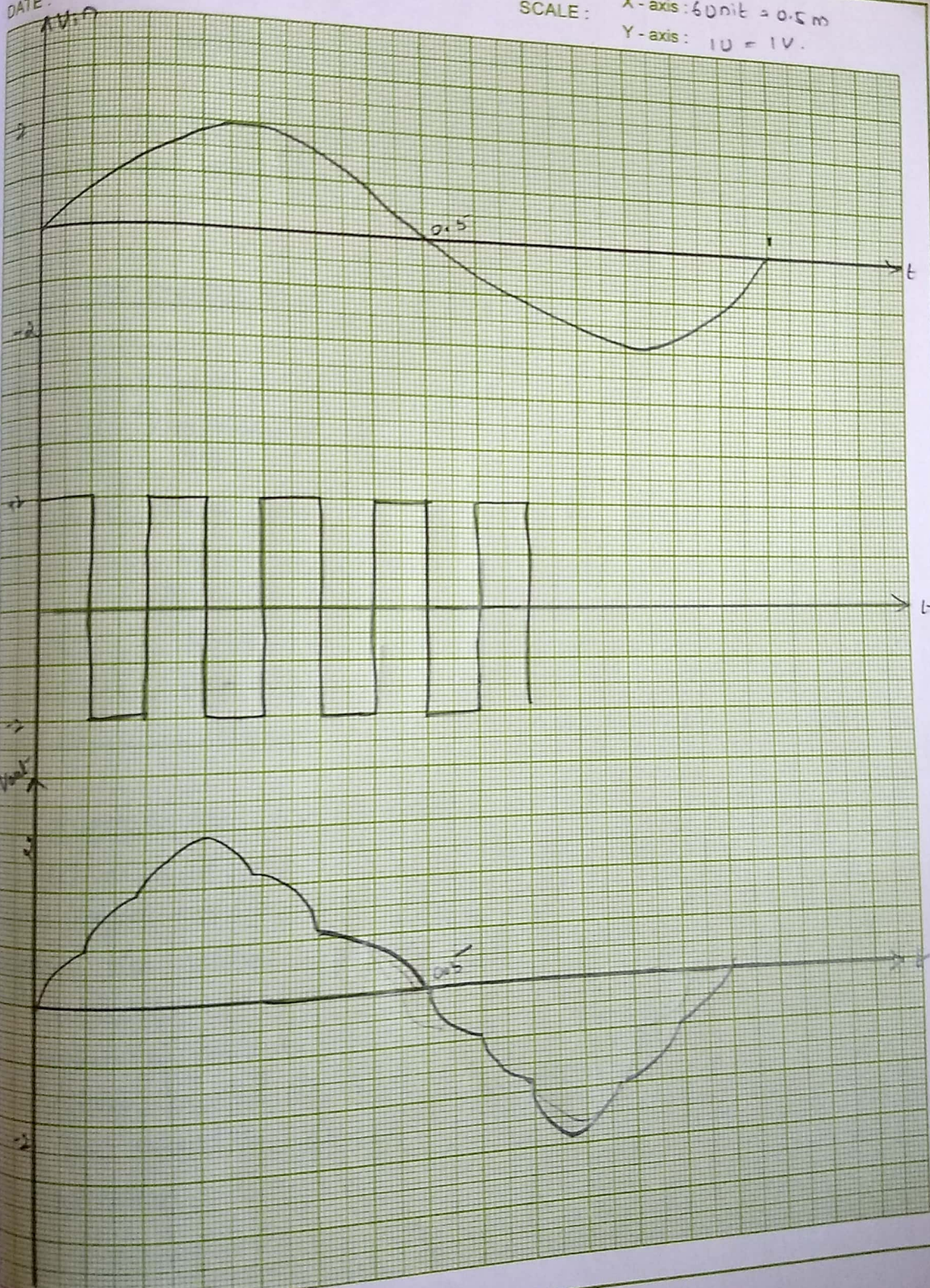SCALE: X-axis: 60 unit = 0.5 m
Y-axis: 10 = 1 V.



5.1 TITLE OF THE EXPERIMENT.

Digital to Analog converter.

5.2. AIM OR OBJECTIVE.


To design and implement a circuit which converts a digital to Analog signal.

5.3. LIST OF COMPONENTS.

S.No.	Components	Specifications	Quantity
1	Regulating Dc	0-20V, 2A.	2
2	CRO	80 Vpp [20MHz]	1
3	Power pack	+12V, -12V.	1
4	op-amp	μA741	1
5	function generator	0-1 MHz.	1
6	Resistors	10k, 1k, 1/2 watt	2, 2
7	BNC Probes	-	2
8	Wires.	-	assorted

5.4. THEORETICAL BACKGROUND.

In electronics, a digital to analog converter is a system that converts a digital signal into an analog signal. An analog to digital converter performs the reverse function. There are several DAC architectures, the suitability of a DAC for a particular application is determined by figures of merit including resolution. Maximum sampling frequency and others. Digital to Analog conversion can degrade a signal so a DAC should be specified that has insignificant errors in terms of the application.

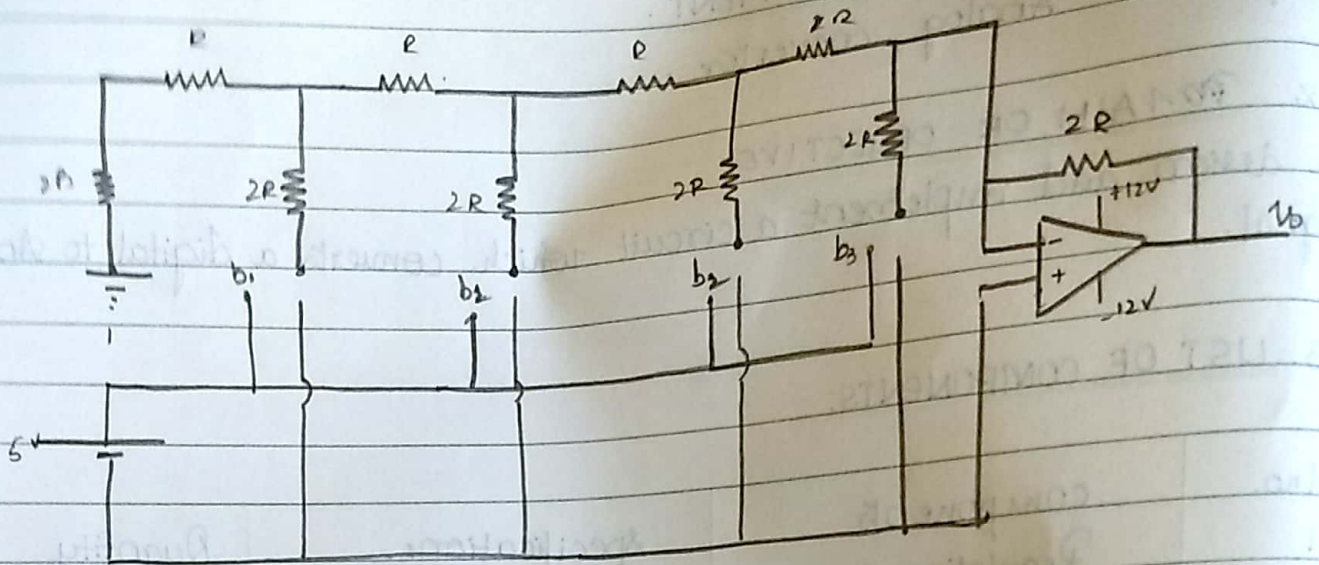DESIGN5.6. PROCEDURE.

- Convert the circuit as shown in the figure.
- Apply the Sinusoidal input of $V_{in} = 2V$ and $f = 1kHz$.
- Take V_{cc} as 5V, $R_f = 10k\Omega$ & assume $R = 34k\Omega$ and construct the resistors according to the circuit.

Repeat the procedure for all possible 4 bit number combinations.
Note down the corresponding Output Voltage

5.7. TABLE OF OBSERVATION

Binary Inputs				$V_o(\text{Calc})$	$V_o(\text{Cal})$	Error
b_3	b_2	b_1	b_0			
0	0	0	0	0	0	0
0	0	0	1	0.552	0.625	0.073
0	0	1	0	1.2	1.25	0.05
0	0	1	1	1.75	1.875	0.125
0	1	0	0	2.5	2.5	0
0	1	0	1	3	3.125	0.125
0	1	1	0	3.7	3.75	0.05
0	1	1	1	4.27	4.375	0.105


Binary Inputs				V_o (obs)	V_o (cal)	Error
b_3	b_2	b_1	b_0			
1	0	0	0			
1	0	0	1	5.2	5	0.2
1	0	1	0	5.75	5.625	-0.125
1	0	1	1	6.4	6.25	-0.15
1	1	0	0	6.46	6.875	-0.085
1	1	0	1	7.72	7.5	-0.22
1	1	1	0	8.27	8.125	-0.145
1	1	1	1	8.57	8.750	0.18
				8.9	9.375	0.47

6.8. SPECIMEN CALCULATION.

$$V_o = \frac{-R_f}{R_i} (V_{ref}) \left[\frac{b_3}{2} + \frac{b_2}{4} + \frac{b_1}{8} + \frac{b_0}{16} \right]$$

Here, $R = 3.9 k\Omega$.

6.9. NATURE OF GRAPH.

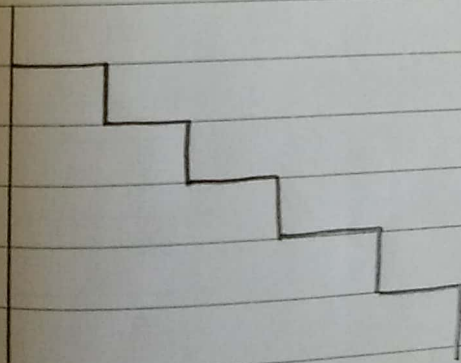

6.10. RESULTS AND CONCLUSION


A digital to analog converter circuit converts a digital signal to an analog signal with resolution of -0.625 for next binary input & corresponding observed & calculated output voltage is noted down.

EXPERIMENT NO. :

DATE :

Page No.:

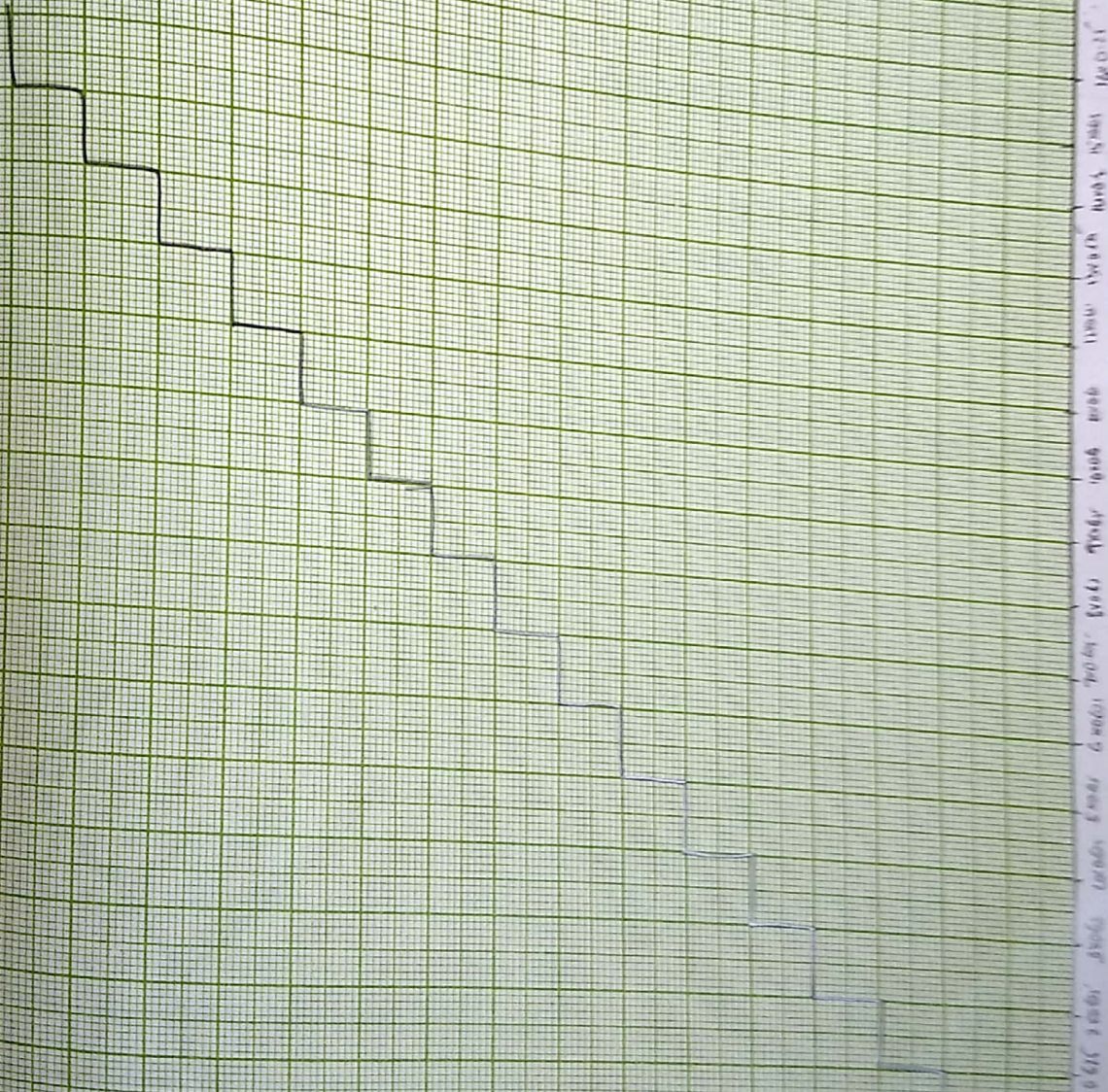SCALE : X - axis : $1U = 0.625V$
Y - axis : $1U = 1cm$



6.1. TITLE OF THE EXPERIMENT


Instrumentation Amplifier.

6.2. AIM OF THE EXPERIMENT.

to design and implement an instrumentation amplifier using INA114

6.3. LIST OF COMPONENTS.

S/no.	components/equipments	Specifications	Quantity
1	Regulated Dc	0-20V, 2A	2
2	Resistors.	1k Ω , 10k Ω 1/2 watt	2, 1
3	DAB	0.1M Ω	1
4	INA114	8 pin	1
5	DMM	-	1
6.	Wires	-	assorted

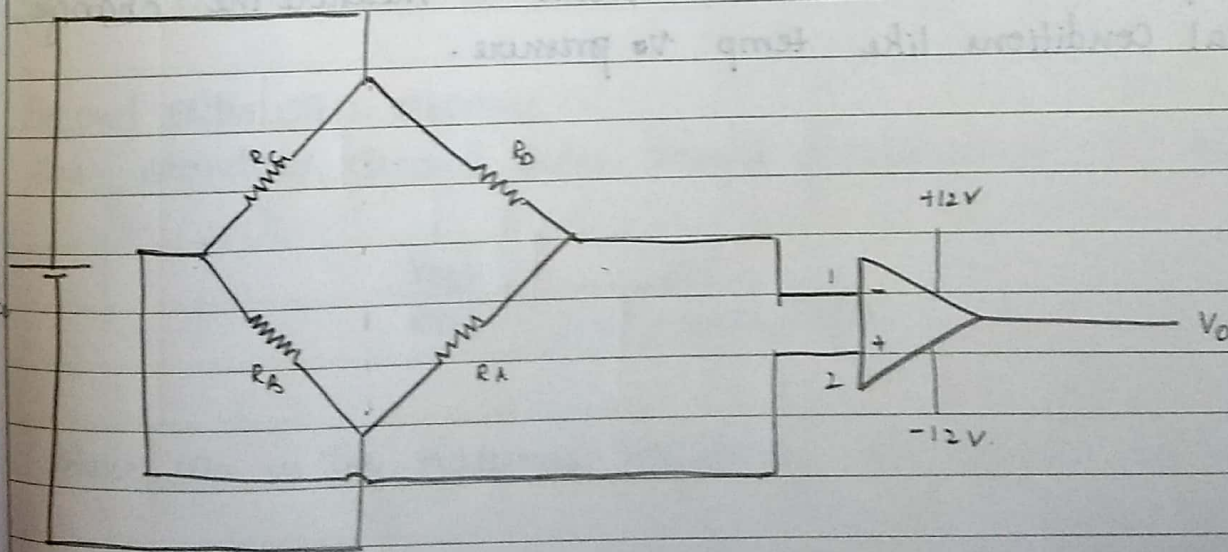6.4. DESIGN

6.5. STEP BY STEP PROCEDURE.

- Make the connections as shown in figure
- Go on Varying R_D and measure V_A & V_B at pin 2 & 3
- Write down Voltages at Pin 6 using DMM.

6.6. TABLE OF OBSERVATIONS.

S.No.	Resistance(Ω)	V_A	V_B	$V = V_A - V_B$	$V_0 = V_G$	V_o	Error
1	3.9k	2.5	2.5	0	0	0	0
2	4k	1.85	1.8	0.05	0.3	0.11	0.19
3	4.1k	1.84	1.8	0.04	0.24	0.18	0.06
4	4.2k	1.82	1.78	0.04	0.24	0.24	0.0
5	4.3k	1.81	1.75	0.06	0.36	0.31	0.05
6	4.4k	1.82	1.75	0.07	0.42	0.38	0.04
7	4.5k	1.78	1.7	0.08	0.48	0.44	0.04
8	4.6k	1.76	1.67	0.09	0.54	0.50	0.04
9	4.7k	1.75	1.65	0.1	0.6	0.55	0.05

6.7. RESULTS AND CONCLUSION.

In the experiment we can use this circuit to measure the change in physical conditions like temp & pressure.

MATLAB EXPERIMENTS.9A.1 TITLE OF THE EXPERIMENT

Second Order step response, peak time Over shoot and unity feedback

9A.2. AIM/OBJECTIVE.

To study and Understand about the Second Order standard transfer function, the maximum Value of the given response to study about the Unity feedback control loops.

9A.3 LIST OF EQUIPMENTS.

S/no	components	specification	Quantity
1	Qube-Servo closed	-	1
2	Quarc controller	-	1
3	Software Simulink	-	1
4	Desktop	-	1

9A.4 THEORETICAL BACKGROUND

Second order step response:

The standard Second Order transfer function has the form


$$\frac{V(s)}{R(s)} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

where ω_n is the natural frequency and ζ is damping factor.

consider Second-Order systems shown in equation (1) subjected to a Step input given by,

$$R(s) = \frac{R_0}{s}$$

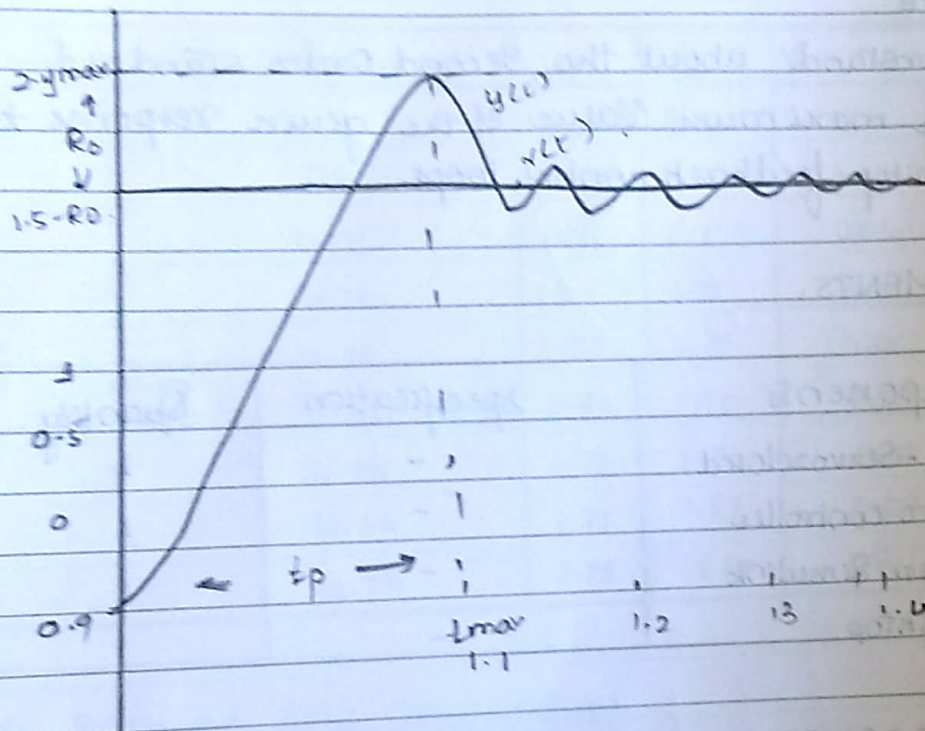where step modulation amplification of $R_0 = 1.5$. The system response to this input shown in fig. whether there is trace output response on $y(t)$ & the dotted trace input is step input.



b) Peak time and Over shoot

The maximum value of the is denoted by Variable y_{max} & it occurs at time t_{max} . For a response similar to figure in previous, the percent Over shoot is found using


$$P_o = \frac{100 (V_{max} - R_0)}{R_0}$$

$$\text{We also have } P_o = 100 e^{\frac{-\sqrt{\lambda} \xi}{1-\xi^2}}$$

$$t_p = \frac{\sqrt{\lambda}}{\omega_n(1-\xi^2)}$$

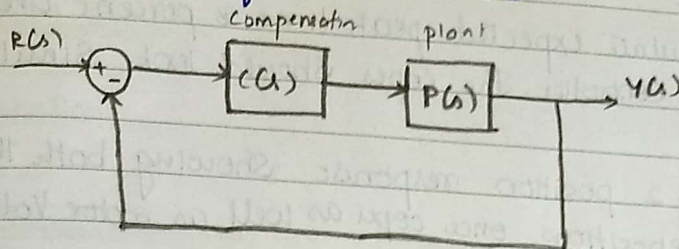c) Unity feedback.


The unity feedback controller loop in the figure will be used to control the position of QUBE-SERVO2



$$P(s) = \frac{\ominus m(s)}{V_m(s)} = \frac{k}{s(Ts+1)}$$


The closed loop transfer function of position control from the reference point $R(s) = \Theta_d(s)$ to output $Y(s) = \Theta_m$ using the feedback.

$$\frac{\Theta_d(s)}{V_m(s)} = \frac{k}{s^2 + \frac{1}{T}s + \frac{k}{T}}$$

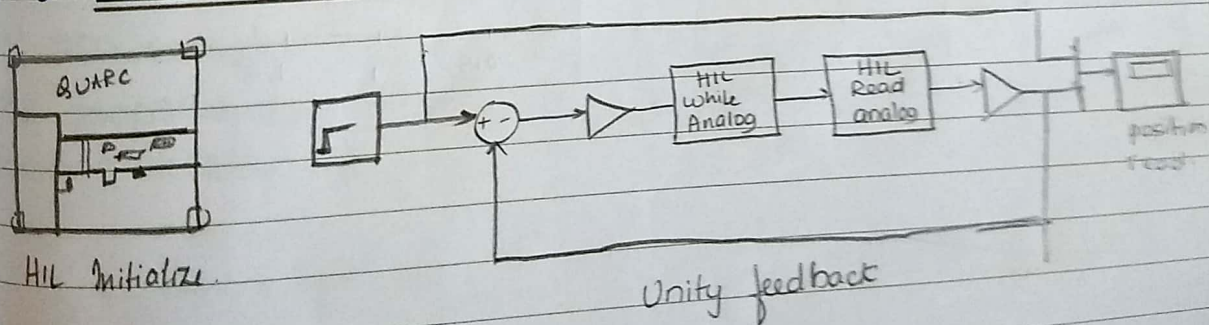9A.5. BLOCK DIAGRAM.

9A.5 DESIGN STEPS

- Given the QUBE-SERVO2-closed loop equations, find natural frequency and damping ratio.
- Based on ω_n & ζ , calculate expected peak time & percent overshoot.
- Build & run the QUARC Controller. The copies should look similar to figure before.
- Attach the cube SERVO 2 position response showing both the Set point and measure depositions once copy as well as motor Voltage.
- Measure the peak time & percent Over shoot from response and compare that with expected results.
- Stop the QUARC controller.
- Power off the servo 2.

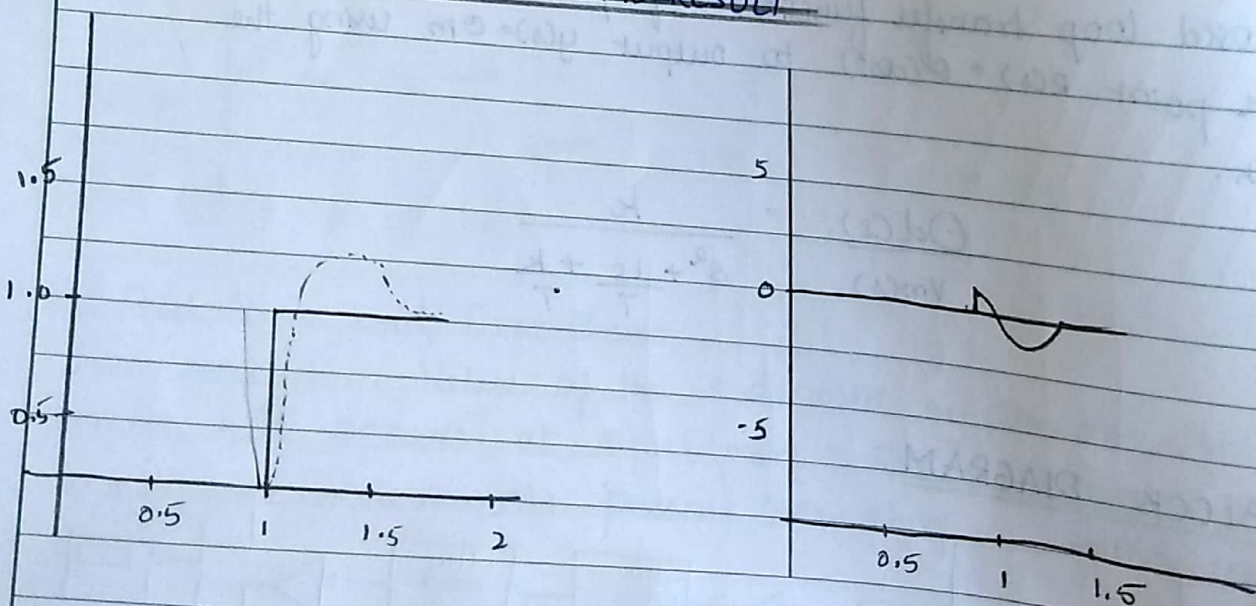9A.7. OUTPUT WAVEFORM AND RESULT

TITLE OF THE EXPERIMENT

Study of Servo model, PID control & PV position control

AIM OF THE EXPERIMENT

The aim is to learn about Servo position control, proportional derivative compensation and designing control according to specifications.

LIST OF THE EXPERIMENTS

Sl. No.	components	Quantity
	QUBE-SERVO(2) closed.	1
	QVARC controller	1
	Simulink Software	1

THEORETICAL BACKGROUND

Servo model.

The QUBE-Servo2 Voltage to position transfer function

$$P(s) = \frac{\theta_m(s)}{V_m(s)} = \frac{k}{s(s+1)}$$

PID control


The proportional, integral & derivative control can be expressed mathematically as,

$$V_c(t) = k_p e(t) + k_i \int e(\tau) d\tau + k_d \frac{de(t)}{dt}$$

The corresponding block diagram is given below.


The controller equation can also be described as,

$$C(s) = k_p + \frac{k_i}{s} + k_d s$$

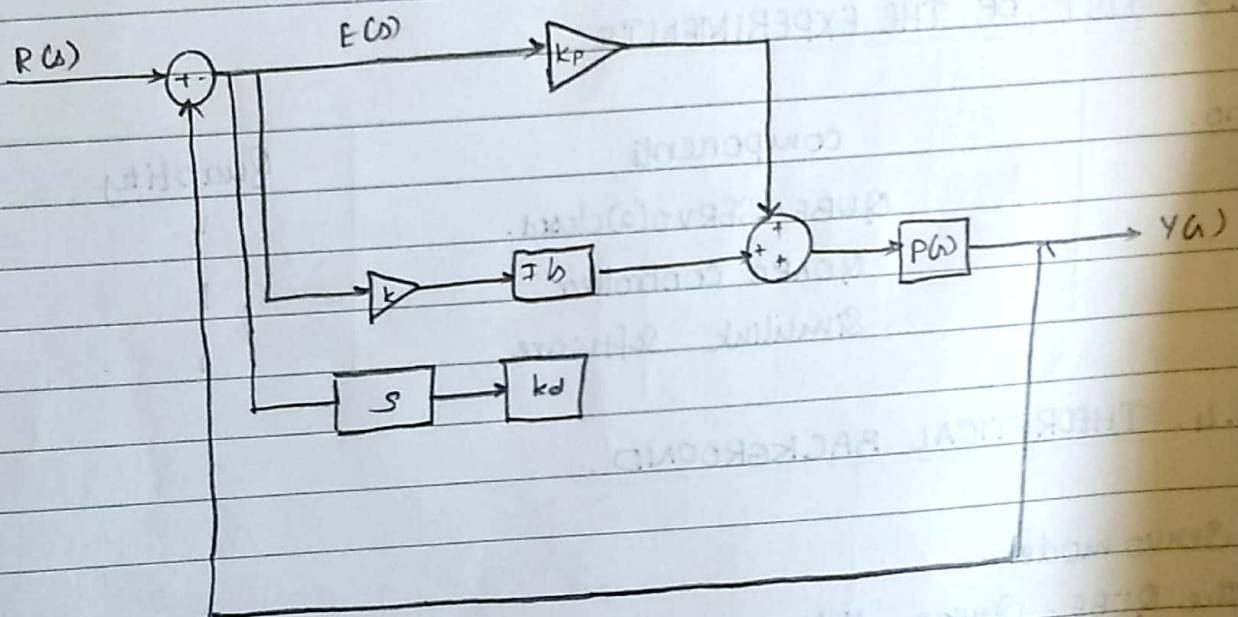

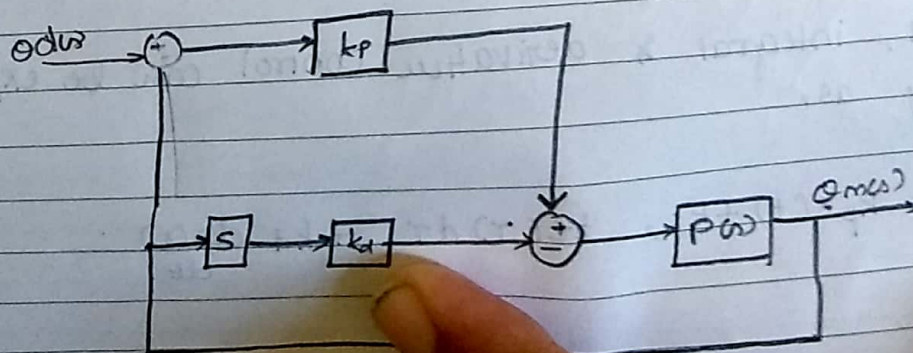c) PV position control

The integral term will not be used to control these server positions. A Variation of the classic PD Control will be used.



Servo 2 is denoted by $y(s)/R(s) = \Theta_m(s)/V_d(s)$. Assume initial $\Theta_m(0^-) = 0$ & $\Theta_m'(0^-) = 0$.

$$V(s) = K_p(R(s) - y(s)) - K_d s y(s)$$

Solving for $y(s)/R(s)$ the obtained loop expression is,

$$\frac{y(s)}{R(s)} = \frac{K_{kp}}{T_s' + (1 + K_{kd})s + K_{kp}}$$


This is the form of 2nd order transfer equation function

$$\frac{y(s)}{R(s)} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$



9B.5 DESIGN STEPS

- Build and run QUARC controller
- Set $K_p = 2.5 \text{ V/rad}$ & $K_d = 0 \text{ V/(rad/s)}$
- Set $K_p = 2.5 \text{ V/rad}$ & Vary derivative gain
- Stop the Quarc controller
- Power OFF QUBE SERVO-2

9B.6 DESIGN

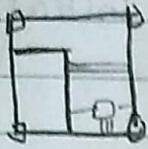

HIL Initialize

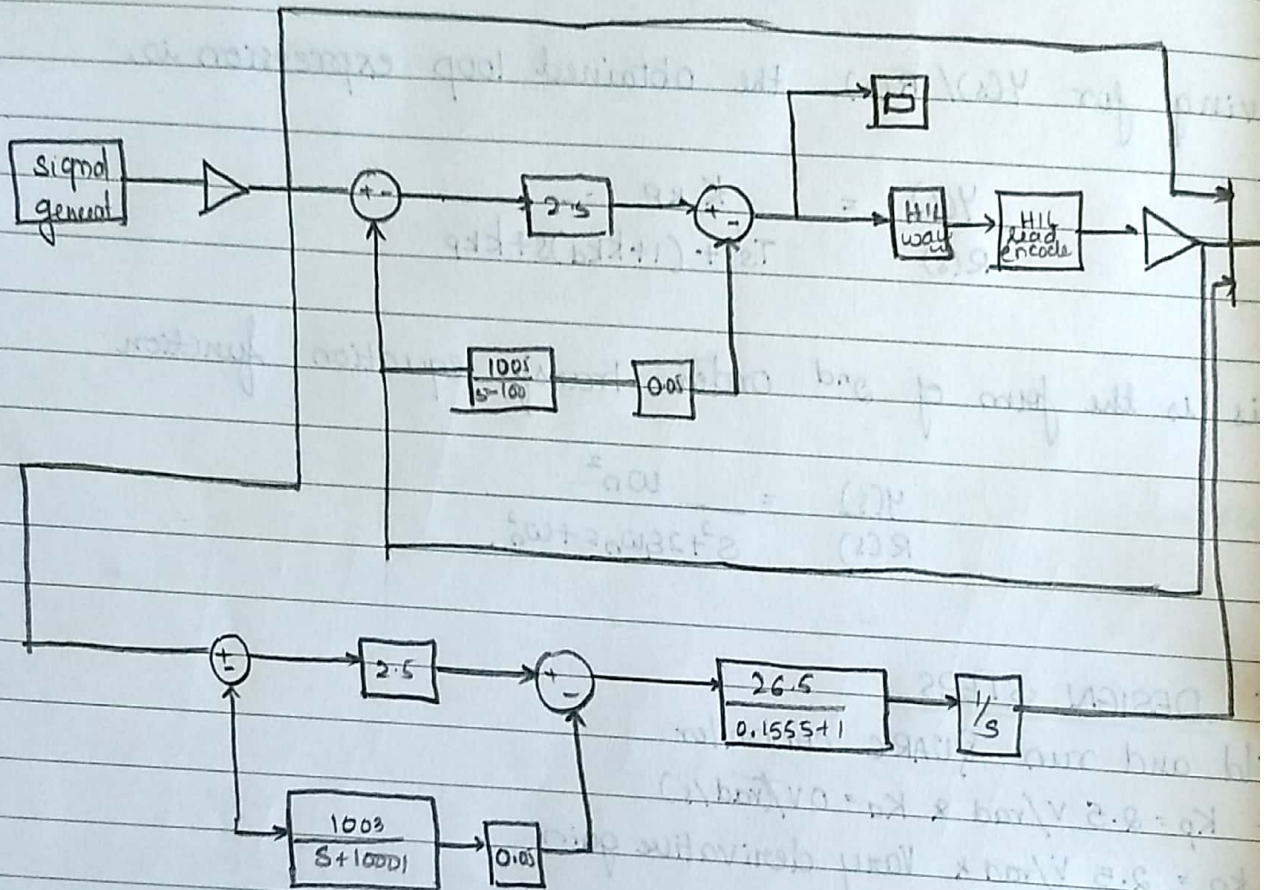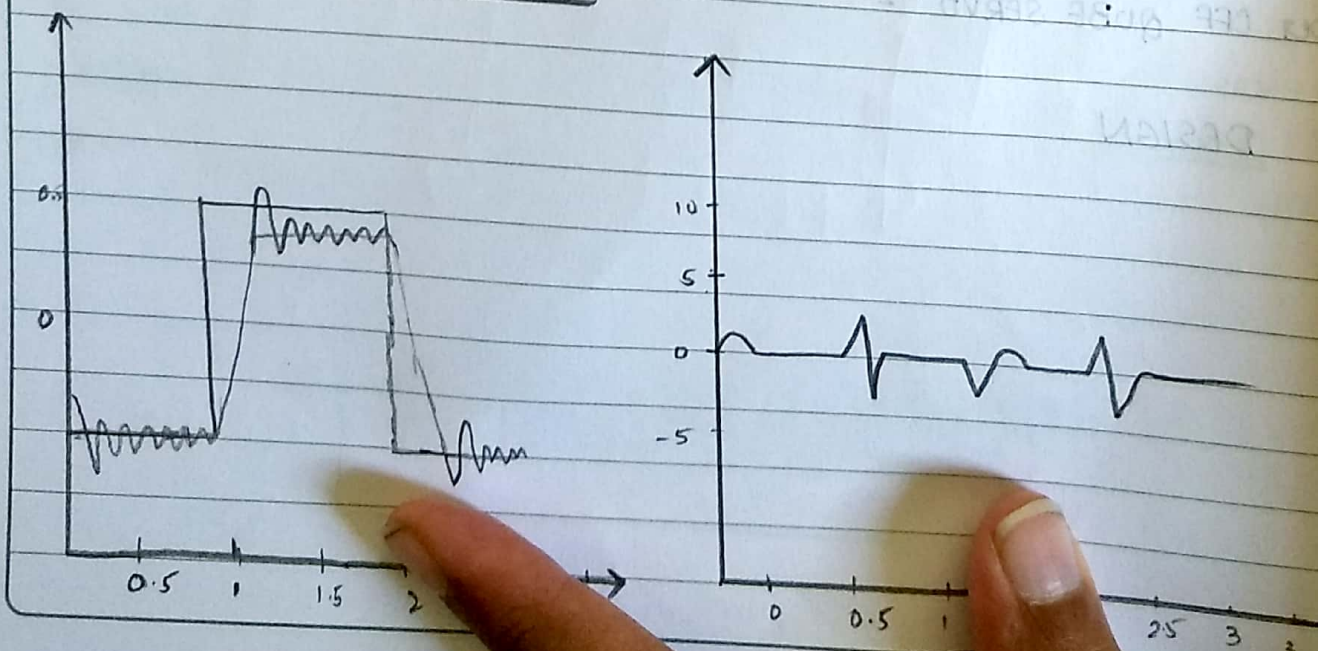98.7 RESULT & WAVEFORM

QC.1. TITLE OF THE EXPERIMENT

Filtering

QC.2. AIM OF THE EXPERIMENT

To study about measuring speed using encoder and to Understand high frequency low pass filters blocking technique.

QC.3. LIST OF EQUIPMENTS

S.No.	Components	Specifications	Quantity
1	GUBE, SERVO 2 closed	-	1
2	QUARC controller	-	1
3	Software Simulink	-	1

QC.4. THEORETICAL BACKGROUND

All low pass filters can usually be used to block out the high frequency components of a signal.

A first order low pass filter transfer function is of the form

$$G(s) = \frac{\omega_f}{s + \omega_f}$$

where, ω_f is the cut off frequency of the filter in radian per second.

QC.5. DESIGN

Take the model and develop into the GUBE-SERVO 2 integration lab, change the encoder calibration gains to measure the gear position in radians.

Build the simulation diagram.

Set up the Source blocks to output are Step Voltage that goes from 1V to 3V @ 0.4Hz.


Build and run the Quarc controller. Examine the encoder speed response.

Attach Sample response


Stop the Quarc controller

Power off the QUBE-SERVO-2

9c.6. BLOCK DIAGRAM

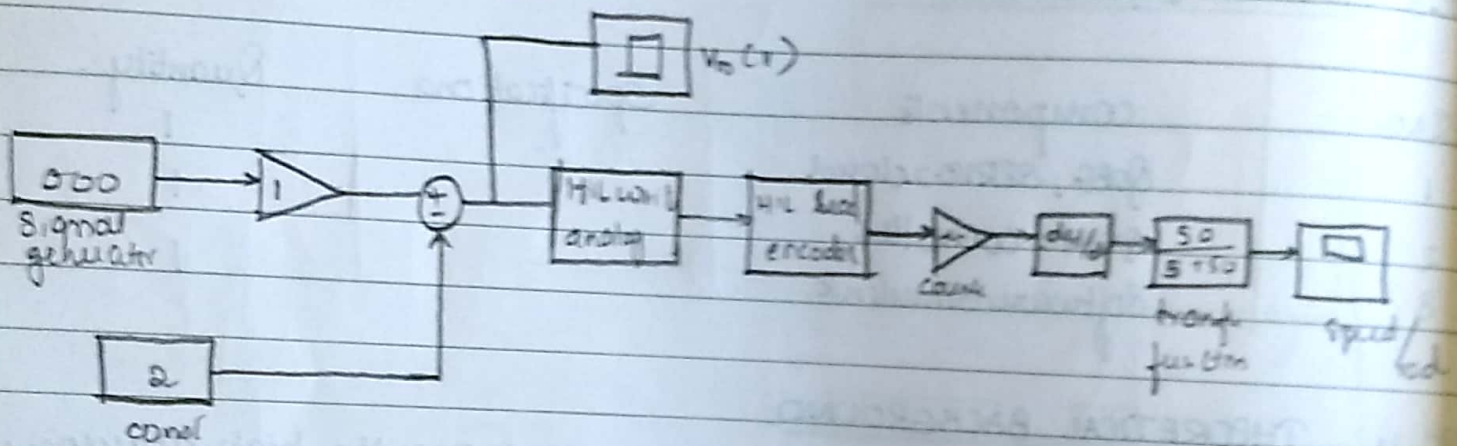

9c.7. OUTPUT WAVEFORM & RESULT

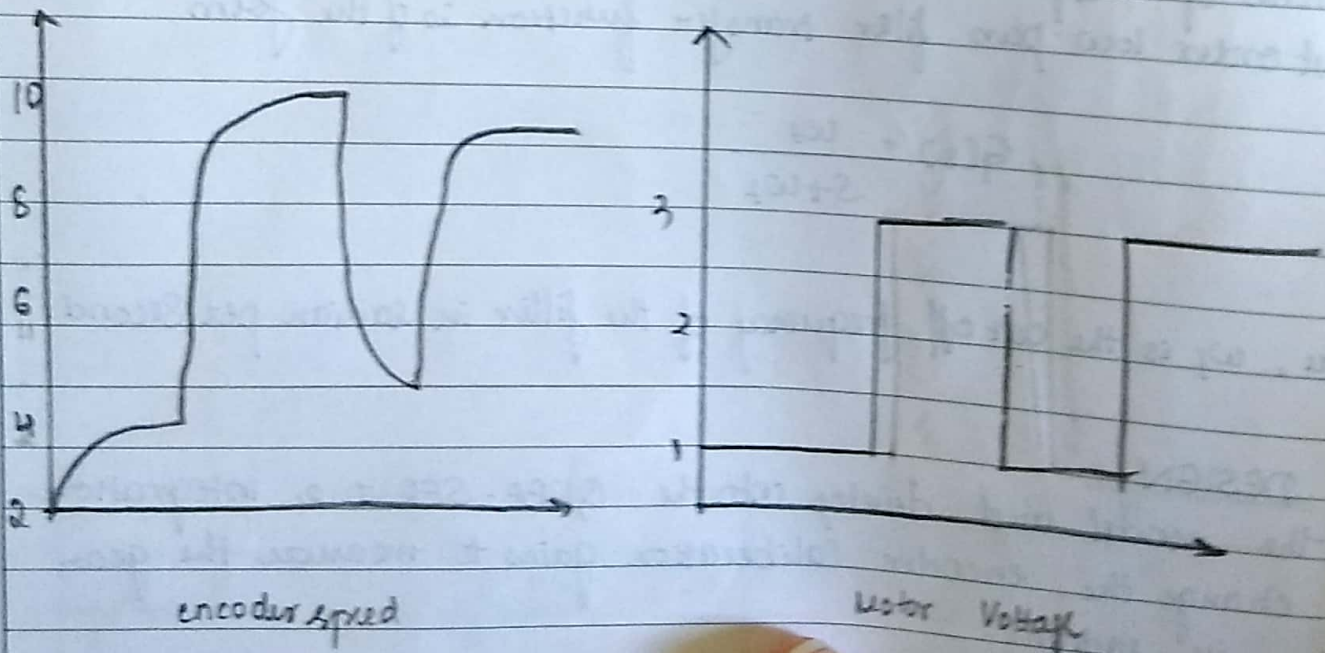

QD.1 TITLE OF THE EXPERIMENT

First principle modelling

QD.2. AIM OF THE EXPERIMENT.

To obtain the equation of a Dc based rotary servo.

To create & validate system model

Model Validation.

QD.3. COMPONENTS REQUIRED

S/no.	components	Quantity
1	QUBE - SERVO2 (closed)	1
2	QUARC controller	1
3	Simulink software	1


QD.4. THEORETICAL BACKGROUND

The Quanser QUBE - SERVO2 is direct

Driver rotary servo system

This motor armature circuit schematic is shown in fig @ below

The electrical & mechanical parameters are given the table

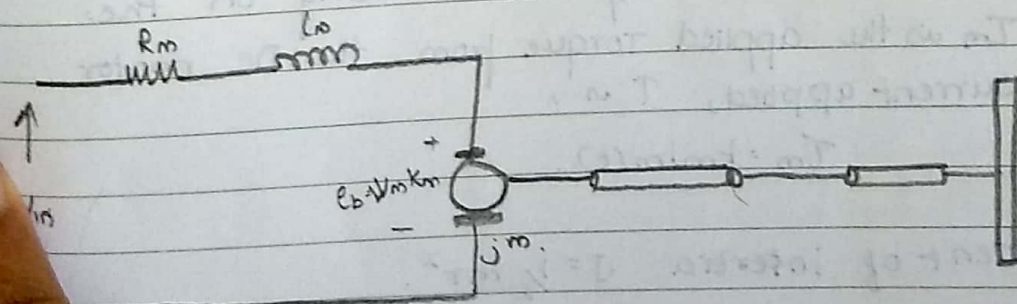The hub is a metal disk used to mount the disk / rotary pendulum and has a moment of inertia of J_h . A disk load attaches to the output shaft with a moment of inertia J_d 

The back-emf (electromotive) voltage $e_b(t)$ depends on the speed of the motor shaft, ω_m & the back-emf constant of the motor, k_m . It opposes the current flow. The back emf voltage is given by,

$$e_b(t) = k_m \omega_m(t).$$

Using Kirchhoff's Voltage law, we can write the following equations.

$$V_m(t) - R_m i_m(t) - \frac{L_m di_m(t)}{dt} - k_m \omega_m(t) = 0. \quad \text{--- (a)}$$

L_m is much less than resistance, it can be ignored.

$$V_m(t) - R_m i_m(t) - k_m \omega_m(t) = 0$$

$$i_m(t) = \frac{V_m(t) - k_m \omega_m(t)}{R_m}.$$

The motor shaft equation is expressed as,

$$J_{eq} \omega_m(t) = T_m(t).$$

where J_{eq} is total moment of inertia acting on the motor shaft and T_m is the applied Torque from the DC motor. Based on current applied, T_m is,

$$T_m = k_m i_m(t).$$

$$\text{Moment of inertia } J = \frac{1}{2} m r^2.$$

DESIGN STEPS

Motor shaft of QUBE-SERVO 2 is attached to lead hub and a disc load based on the parameters given table. Calculate the equivalent moment of inertia that is acting on motor shaft.

Design of QUBE

SERVO-2 motor sub-system described above, attached, Server capture of the model & the matlab script.

Build and run the QUARC controllers with your QUBE

Stop the QUARC controller

Power off the QUBE-SERVO-2.

9D.6 OUTPUT WAVEFORM AND DESIGN